

**III B. TECH I SEMESTER REGULAR EXAMINATIONS, NOVEMBER - 2022**  
**LINEAR IC APPLICATIONS**  
**(Electronics and Communication Engineering)**

Time: 3 Hours

Max. Marks:70

**Note:** Answer **ONE** question from each unit ( $5 \times 14 = 70$  Marks)

UNIT-I


1. a) Draw and explain the circuit diagram of output stage of operational amplifier. [7M]
- b) Explain the operation and working of basic BJT current mirror circuit. [7M]

(OR)

2. a) Draw and explain the internal circuit diagram of intermediate stage of operation amplifier. [7M]
- b) Explain the working of widlar current mirror circuit with a neat sketch. [7M]

UNIT-II

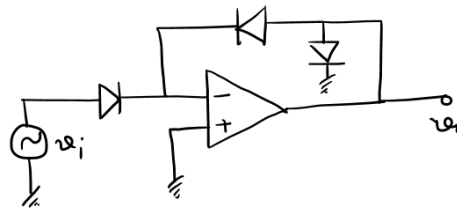3. a) Draw the circuit of inverting integrator and explain its working. [7M]
- b) Consider the following circuit and draw the output waveform. [7M]



(OR)

4. a) Draw and explain the working of op-amp based voltage to current converter. [7M]
- b) Implement the square wave generating circuit using op-amp. [7M]

UNIT-III

5. a) Draw the circuit diagram of second order Butterworth low pass filter using operational amplifier. [7M]
- b) Explain the working and operation of RC phase shift oscillator. [7M]

(OR)

6. a) Draw the circuit diagram of first order Butterworth high pass filter using operational amplifier. [7M]
- b) Draw the circuit diagram of sample and hold circuit and explain its working. [7M]

## UNIT-IV

7. a) Draw the pin diagram of 555 timer and implement an astable multivibrator. Also, find the duty cycle. [7M]

b) Implement a frequency multiplier using PLL. [7M]

(OR)

8. a) Explain the working of voltage-controlled oscillator. [7M]

b) Implement a missing pulse detector using monostable mode. [7M]

## UNIT-V

9. a) Explain the working and operation of successive approximation type ADC. [7M]

b) Explain about binary weighted 3-bit DAC with a neat sketch and plot transfer characteristics. [7M]

(OR)

10. a) Explain the working of dual-slop ADC. [7M]

b) List DAC/ADC specifications and explain. [7M]

\* \* \* \* \*