

I B. TECH II SEMESTER REGULAR EXAMINATIONS, SEPTEMBER - 2021
BASIC CIRCUIT ANALYSIS
(ELECTRICAL AND ELECTRONICS ENGINEERING)

Time : 3 Hours

Max. Marks : 70

Note : Answer ONE question from each unit (5 × 14 = 70 Marks)

UNIT-I

1. a) Define KCL and KVL. Resistors of $R_1 = 10\Omega$, $R_2 = 4\Omega$ and $R_3 = 8\Omega$ are connected to two batteries (of negligible resistance) as shown in Fig.1 Find the current through each resistor [7M]


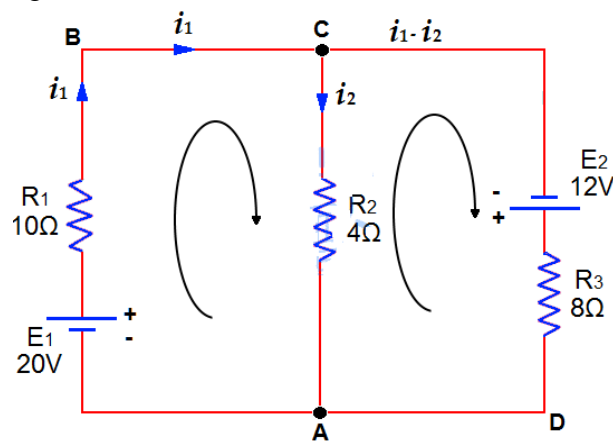


Fig.1

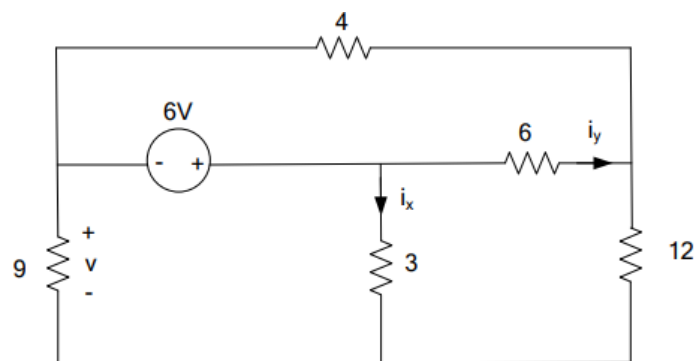- b) Write the mesh (loop) equations for the following circuit and then find i_x , i_y and v . [7M]



(OR)

2. a) Solve for the current flowing through the each resistor in Fig.2 [7M]

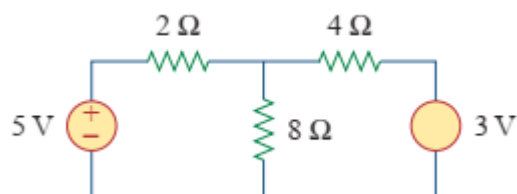


Fig.2

- b) Calculate equivalent resistance across terminals A and B in Fig.3 [7M]

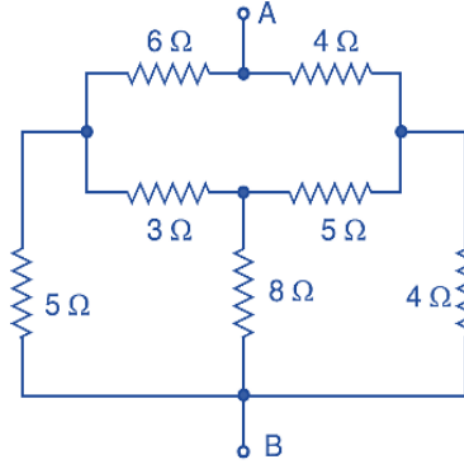


Fig.3

UNIT-II

3. a) Calculate the phase angle between $V_1=10\cos(\omega t+50)$ and $V_2=12\sin(\omega t-10)$. [4M]
State which sinusoid is leading.
- b) Explain concept of admittance? And explain parallel RL circuit across sinusoidal supply. [10M]

(OR)

4. a) Explain the following terms (i) Peak value (ii) Average value and (iii) RMS value [7M]
- b) The current in a circuit lag the voltage by 30° . If the input power be 400W and the supply voltage be $V=100\sin(370t)$. Find the complex power [7M]

UNIT-III

5. a) Find I_o in Fig.4 using mesh analysis [7M]

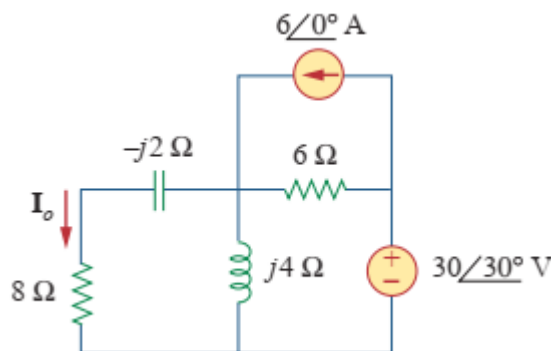


Fig.4

- b) If a series of LCR circuit has same current at $\omega=100$ rad/sec, and $\omega=900$ rad/sec, then find resonance frequency in Hz of the circuit. [7M]

(OR)

6. a) Define Resonance also derive the condition for resonance in a series RLC circuit. [7M]
- b) Write a short notes on (i) Selectivity (ii) Bandwidth. [7M]

UNIT-IV

7. a) Find the Thevenin's equivalent circuit across the terminals ab shown in Fig.5 [7M]

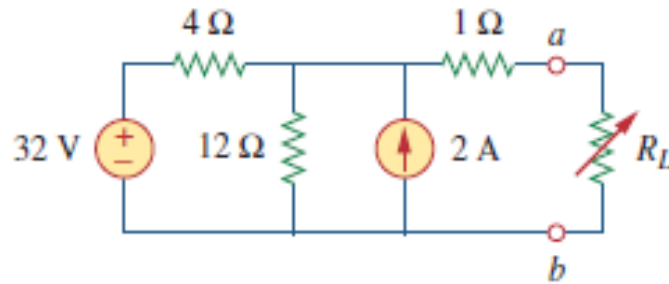


Fig.5

- b) Verify the Reciprocity theorem in the circuit shown in Fig.6 [7M]

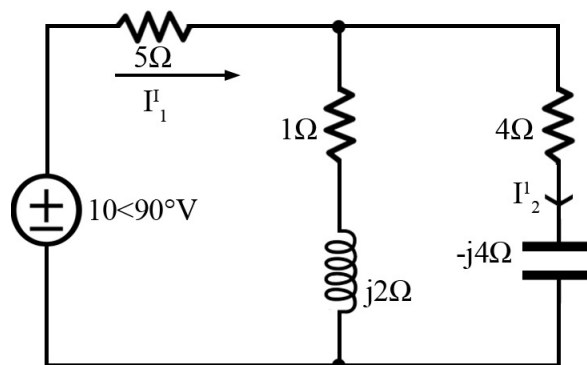


Fig.6

(OR)

8. a) Find the current through 10 Ω resistance in the given network shown in Fig. 7 [7M] by using Superposition theorem

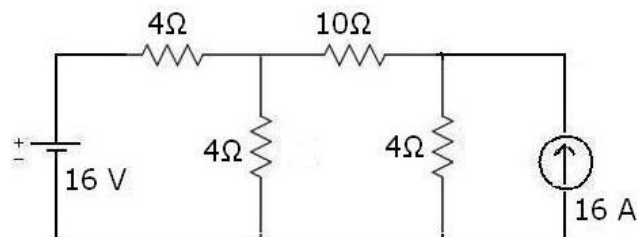


Fig. 7

- b) Find the current and voltage across the load terminal shown in Fig. 8 using Millman's theorem [7M]

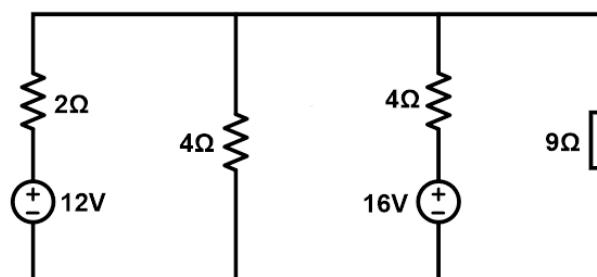


Fig.8

UNIT-V

9. a) Show that in a series magnetic circuit total reluctance equals to sum of individual reluctances. [7M]
 b) Calculate the phasor currents I_1 and I_2 in the circuit of Fig.9. [7M]

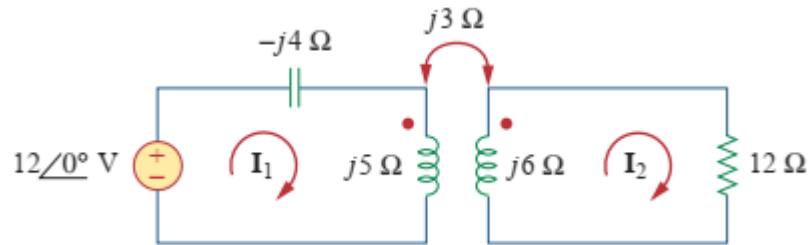


Fig.9

(OR)

10. a) Explain the following terms (i) Magnetic Field, (ii) Magnetic Flux, (iii) Magnetic Flux Density. [7M]
 b) Determine the M.M.F. required to generate a total flux of $100\mu\text{Wb}$ in an air gap 0.2 cm long. The cross-sectional area of the air gap is 25 cm^2 . [7M]
