

I B.TECH II SEMESTER REGULAR EXAMINATIONS, SEP - 2021
NETWORK ANALYSIS
(ELECTRONICS AND COMMUNICATION ENGINEERING)


Time: 3 Hours

Max. Marks: 70


Note: Answer **ONE** question from each unit ($5 \times 14 = 70$ Marks)

~~~~~  
 UNIT-I

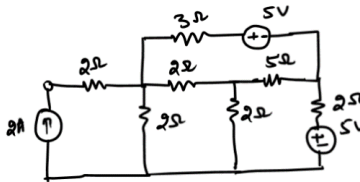1. a) Calculate the current in each branch of the following network. [7M]




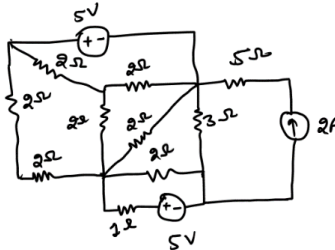- b) Find the current in each branch of the following network. The star-delta transformation must be utilized in the analysis. [7M]




(OR)

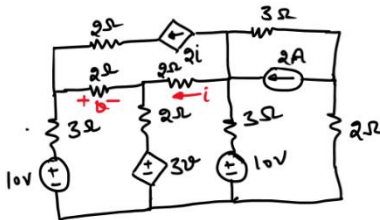2. a) Find the current in each branch of the following network using nodal analysis. [7M]




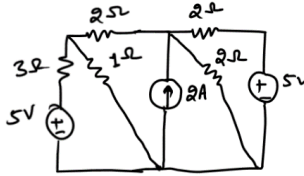- b) Calculate the voltage across all the resistances of the following [7M] network using Mesh analysis.




## UNIT-II

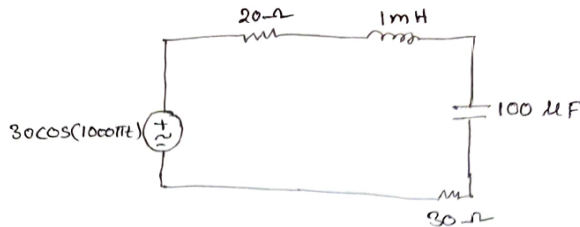3. a) Find the current in the following circuit thus find the power [7M] supplied by the source.




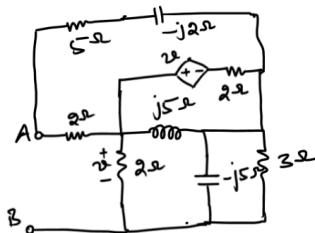- b) Calculate the equivalent impedance of the following network [7M] across the terminals A-B.




(OR)

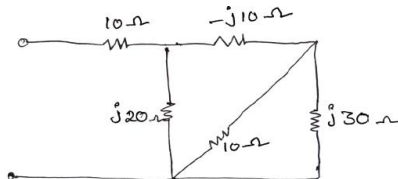4. a) Find the impedance between terminals a and b in the following [7M] circuit.




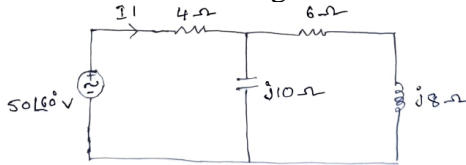b) Find the current  $I_1$  in the following ac circuit. [7M]




### UNIT-III

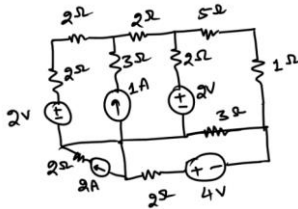5. a) Apply the superposition theorem and find the current in each branch of the following network. [7M]



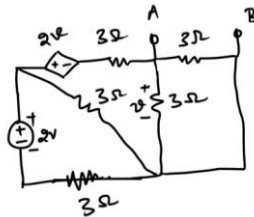
b) Find the Norton's equivalent circuit across the terminal AB. [7M]



(OR)


6. a) State and prove the Thevenin's theorem by taking an example. [7M]

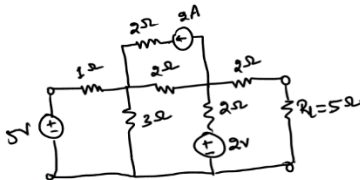b) Find the maximum power transferred to the load of  $5\Omega$  given in the following network. [7M]




### UNIT-IV

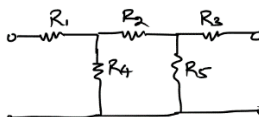7. a) Make the ABCD-parameter model of the following network. [7M]




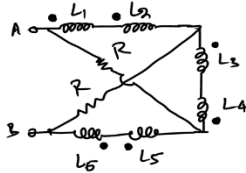- b) Find the equivalent impedance of the following network. [7M]




(OR)

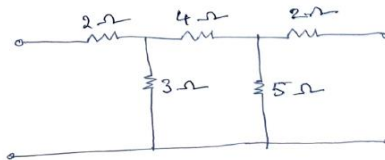8. a) Convert the  $Y$ -parameters to transmission parameters. [7M]  
 b) Find the  $Z$ -parameters of the following network. [7M]




UNIT-V

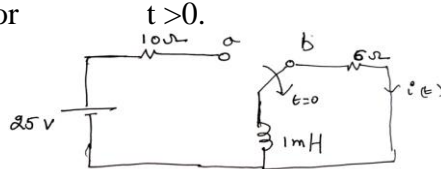9. a) Explain initial and final (steady state) behaviours of  $R$ ,  $L$  and  $C$  for the dc excitation. [7M]  
 b) In the following circuit the switch is moved from a to b at  $t = 0$ . Find  $i(t)$  for  $t > 0$ . [7M]



(OR)

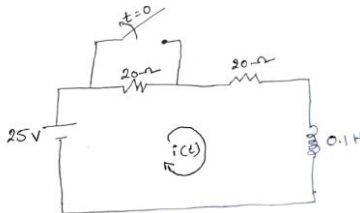10. a) Obtain the voltage across capacitor for  $t > 0$  in the first order series  $RC$  circuit when the DC voltage  $V$  applied at  $t = 0$ . Assume all initial conditions to be zero. [7M]  
 b) In the following circuit the switch is opened at  $t = 0$ . Determine the expression for  $i(t)$  for  $t > 0$ . [7M]



\*\*\*\*\*